

End Semester Examinations - 2015-16 Even Semester - May 2016

14EC1001 Basic Electronics Engineering

Set B

Time : 3 hrs
Total Marks: 100

-
1.
 - a. Explain the various types of an inductor. (10)
 - b. Explain about the carbon film resistors and trimmer with suitable diagrams. (10)
 - OR**
 2.
 - a. Explain the formation of P-type semiconductor through the covalent bond structure. (10)
 - b. Using the colour coding table, find the resistance value for the following (10)
 - a. Red, Red, Black, Gold
 - b. Green, Red, Black, Silver
 - c. Yellow, Red, Red, Gold
 - d. Red, Green, Black, Gold
 3.
 - a. Explain the input and output characteristics of common emitter configuration of a BJT(14).
 - b. Compare the CB, CE, and CC configurations. (6)
 - OR**
 4.
 - a. Explain the working principle of half wave rectifier. (10)
 - b. Draw the circuit of Zener voltage regulator and explain its working. (10)
 5.
 - a. Simplify using 4-variable K-map (6)
 $\Sigma m(0,1,2,3,4, 5,6,7,8,9,10,11)$
 - b. Explain the working of 4x1 data selector and 1x4 data distributor. (14)
 - OR**
 6.
 - a. Prove the following: (6)
(i) $A+A'B = A+B$; (ii) $AB + A'C + BC = AB + A'C$; (iii) $A+AB = A$
 - b. Implement the basic logic gate functions using universal gates (14)
 7.
 - a. Derive the expression for frequency modulation. (14)
 - b. Explain the need for modulation. (6)
 - OR**
 8.
 - a. Explain the working of FM transmitter with a block diagram. (10)
 - b. Explain the working of superheterodyne receiver with a block diagram. (10)
 9.
 - a. Explain the working of Optical Fibre Communication with its block diagram. (10)
 - b. Explain the working of Radar system with its block diagram. (10)
-

Wishing you All the Best
